

CS226 Project Report

IITB-Proc

Dhruv Arora - 190050034
Raj Aryan Agrawal - 190050097
Sahasra Ranjan - 190050102
Sibasis Nayak - 190050115

May 21, 2021

Final Circuit

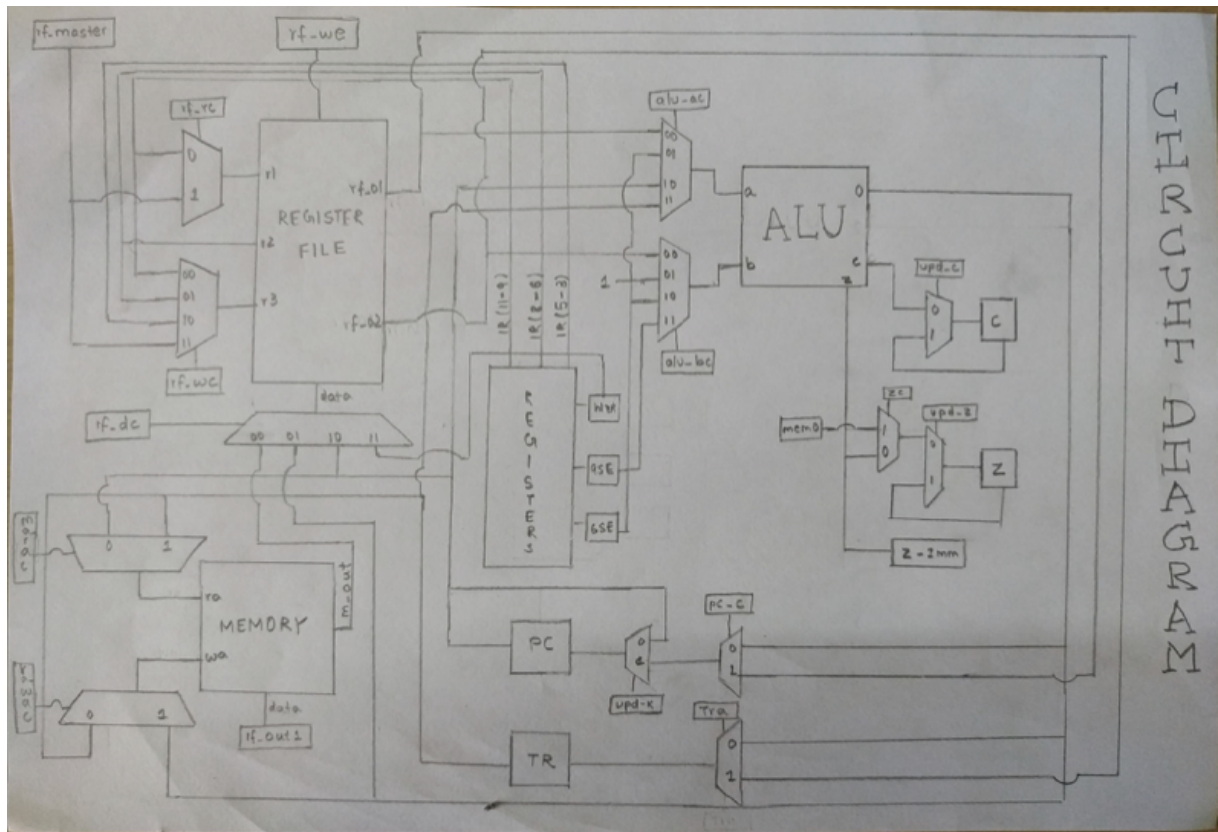


Figure 1: Final Circuit

State Transition Diagram for FSM

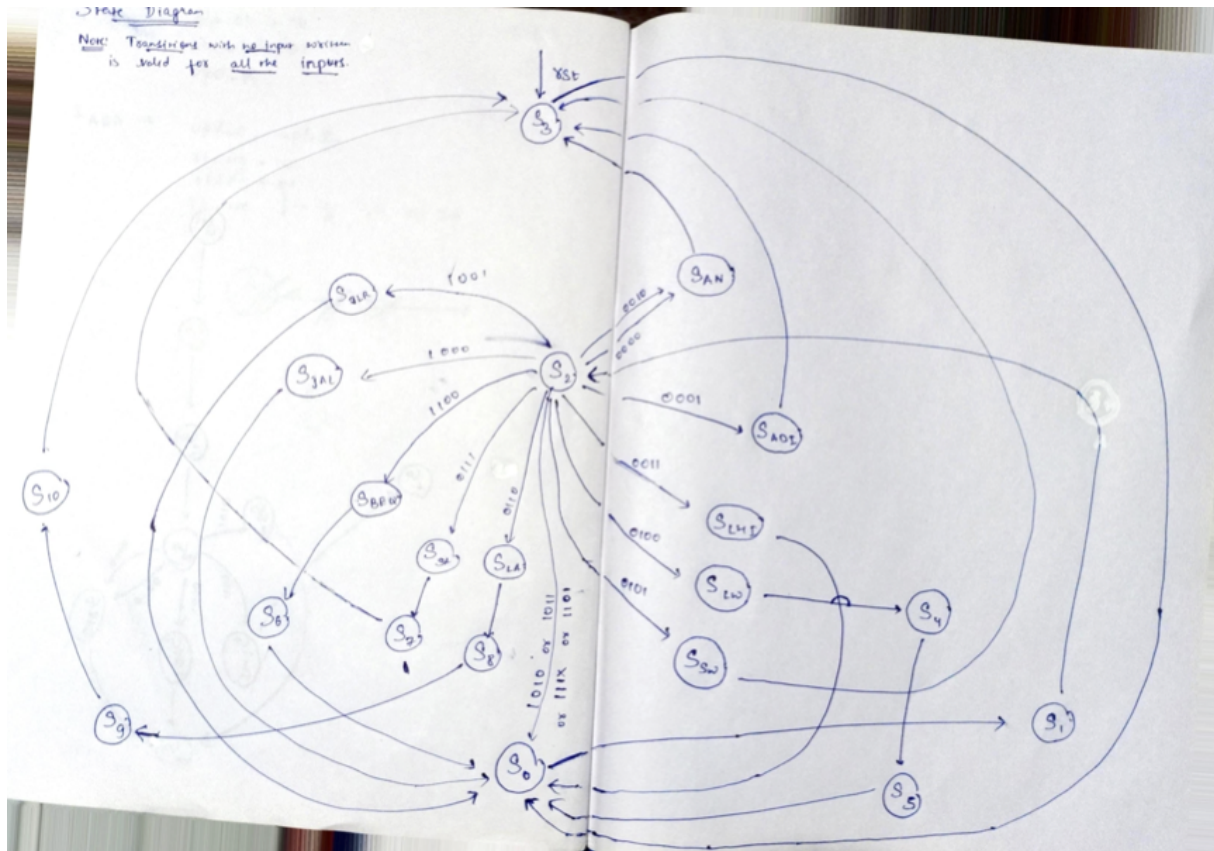


Figure 2: State Transition Diagram

States in the FSM

1. S_0 : State for synchronization. Next state: S_1
2. S_1 : Update instructions
3. S_2 : Understand instruction and proceed to compute in single state instructions. Set appropriate controls for ADD, ADZ, ...
4. S_3 : If a single state transition, reset the FSM.
 - $alu_ac = 10$
 - $alu_bc = 01$
 - $upd_pc = 1$
5. S_4 : Activate memory read control
 - $m_rac = 1$
6. S_5 : Reset the FSM (for LW operation)
 - $rf_we = 1$
 - $zc = 1$

- upd_pc = 1
 - alu_ac = 10
 - alu_bc = 01
7. S_6 : Final state for BEQ operation, change the branch accordingly and reset the FSM
- alu_ac = 10
 - upd_pc = 1
 - if z_imm is 1, alu_bc is set to "10" else is set to "01"
8. S_7 : For SA operation
- rf_rc = 1
 - m_we = 1
 - alu_ac = 11
 - alu_bc = 01
9. S_8 : For LA operation read instruction from memory
- m_rac = 1
 - alu_ac = 11
 - alu_bc = 01
10. S_9 : For LA update writing controls
- m_rac = 1
 - alu_ac = 11
 - alu_bc = 01
 - rf_we = 1
 - rf_wc = 11
11. S_{10} : For LA update the register and go to state 3
- rf_we = 1
 - rf_wc = 11
12. S_{AN} : Controls for ADD / ADC / ADZ / NDU / NDC / NDZ
- upd_c = 1, upd_z = 1
 - rf_wc = 10
 - rf_dc = 01
 - rf_we = 1
 - alu_op = 1
13. S_{ADI} : Controls for ADI

- $\text{upd_c} = 1, \text{upd_z} = 1$
 - $\text{rf_wc} = 01$
 - $\text{rf_dc} = 01$
 - $\text{rf_we} = 1$
 - $\text{alu_bc} = 10$
14. S_{LHI} : Controls for LHI
- $\text{upd_pc} = 1$
 - $\text{rf_dc} = 11$
 - $\text{rf_we} = 1$
 - $\text{alu_ac} = 10$
 - $\text{alu_bc} = 01$
15. S_{LW} : Controls for LW
- $\text{alu_ac} = 01$
16. S_{SW} : Controls for SW
- $\text{alu_ac} = 01$
 - $\text{alu_a} = 10$
 - $\text{alu_bc} = 01$
 - $\text{m_wac} = 1$
 - $\text{m_we} = 1$
 - $\text{upd_pc} = 1$
17. S_{LA} : Controls for LA
- $\text{trc} = 1$
18. S_{SA} : Controls for SA
- $\text{trc} = 1$
19. S_{BEQ} : Controls for BEQ
- $\text{alu_cin} = 1$
20. S_{JAL} : Controls for JAL
- $\text{rf_dc} = 10$
 - $\text{rf_we} = 1$
 - $\text{alu_ac} = 10$
 - $\text{alu_bc} = 11$
 - $\text{upd_pc} = 1$

21. S_{JLR} : Controls for JLR

- $\text{rf_dc} = 10$
- $\text{rf_we} = 1$
- $\text{pc_c} = 1$
- $\text{upd_pc} = 1$